

Ihsan Doğramacı Bilkent University

CS 224


Computer Organization

**Preliminary Design Report
Lab-4**

**Kerem Ayöz
Section 03 / 21501569**

14/11/2017


Part b

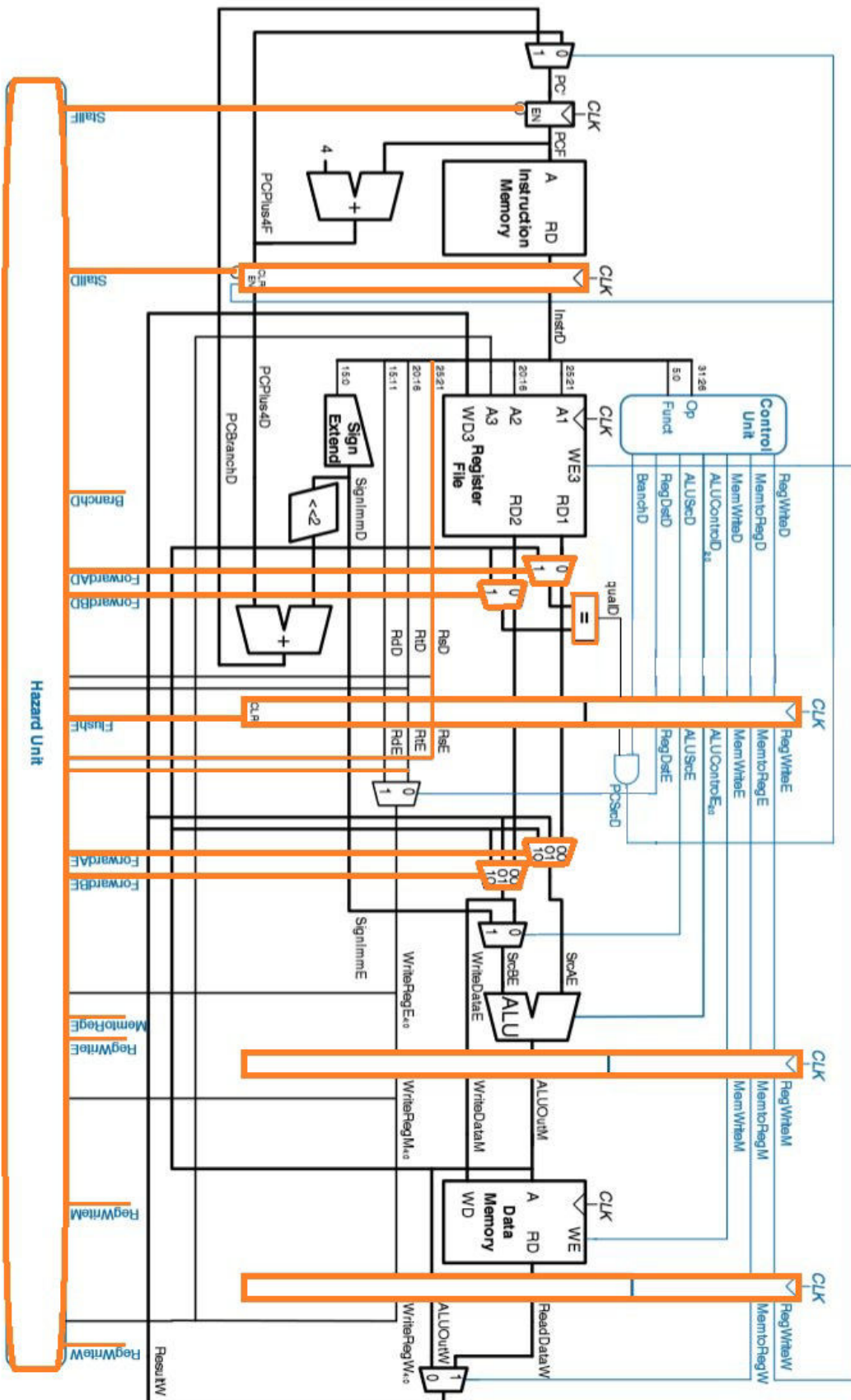

Part c


RAW(Read after Write) Hazards

1- Compute-use

 


Here the *sub* and *and* instructions try to read the value in \$t0 before the add instruction's write operation on \$t0 is completed. This causes a RAW hazard and could be solved by forwarding.

2- Load-use

 

In that type of situations, forwarding is not enough to solve the hazard because the data that the sub and and instructions need could not be written before the time that sub and instructions are in the decode/fetch stage. Therefore, the next two instructions should be stalled and single forwarding to the sub instruction is enough to solve that type of hazard.

3- Load-store

 

In that situation, sw needs the data in \$t0 before it goes into the memory stage. However, the lw instruction completes the write after the memory stage. Therefore, single forwarding is enough for handling the hazard.

Control Hazards

1- J-Type Instructions

```
j Target          IF D EXE MEM WB
sw $t0, 88($t4)   IF D EXE MEM WB
.
.
```

Target: ...

The jump instruction changes the PC and because the address calculation occurs in the decode stage, it should clear whatever the next instruction is. So flushing one instruction is enough for that hazard.

2- Branch Instruction

```
beq $t1, $t0, Target IF D EXE MEM WB
sw $t0, 88($t4)       IF D EXE MEM WB
addi $t0, $t4, 102     IF D EXE MEM WB
.
.
```

Target: ...

As like the jump instruction, next instruction should be cleared but this time if this operation is needed if the branch is taken. Since BTA calculation is done at execute stage, the instructions at decode and fetch stage should be cleared thus 2 flushes needed to handle that type of hazards.

Part d

RAW(Read after Write) Hazards

1- Compute-use

Logic equation

```
if ((rsE != 0) AND (rsE = WriteRegM) AND RegWriteM) then
ForwardAE = 10
else if ((rsE != 0) AND (rsE = WriteRegW) AND RegWriteW) then
ForwardAE = 01
else ForwardAE = 00
```

2- Load-use

Logic equation

```
lwstall = ((rsD = rtE) OR (rtD = rtE)) AND MemtoRegE
StallF = StallD = FlushE = lwstall
```

3- Load-store

Logic equation

```
if ((rsE != 0) AND (rsE = WriteRegM) AND RegWriteM) then
ForwardAE = 10
else if ((rsE != 0) AND (rsE = WriteRegW) AND RegWriteW) then
ForwardAE = 01
else ForwardAE = 00
```

Control Hazards

1- J-Type Instructions

Logic equation

```
if (JumpD == 1) then
FlushE = 1
else
FlushE = 0
```

2- Branch Instruction

Logic equation

```
ForwardAD (rsD != 0) AND (rsD = WriteRegM) AND RegWriteM
ForwardBD (rtD != 0) AND (rtD = WriteRegM) AND RegWriteM

branchstall
BranchD AND RegWriteE AND (WriteRegE = rsD OR WriteRegE = rtD)
OR
BranchD AND MemtoRegM AND (WriteRegM = rsD OR WriteRegM = rtD)

StallF StallD FlushE lwstall OR branchstall
```

Part e

Modules that need to be changed

- Pipeline registers for Fetch, Decode, Execute and Memory stages are added. Parametrized registers are used for every input.
- Equality comparator module added to the decode stage for branch decision.
- Hazard unit and forwarding muxes added.
- 3to1 mux module added to execute stage for forwarding.
- Branch decision AND gate moved to execute stage with PcSrc Signal.
- Zero output removed from ALU.
- Many wires added to support new modules and connections.
- Many wires were renamed to represent stages.

Changes to controller

- Many wires were renamed to represent stages.

Part g

Test program for new instructions

```
addi $v0 $zero 0x0005
addi $v1 $zero 0x000C
addi $a3 $v1 0xFFFF7
or $a0 $a3 $v0
and $a1 $v1 $a0
add $a1 $a1 $a0
beq $a1 $a3 0x000A
slt $a0 $v1 $a0
beq $a0 $zero 0x0001
addi $a1 $zero 0x0000
slt $a0 $a3 $v0
add $a3 $a0 $a1
sub $a3 $a3 $v0
sw $a3 0x0044 $v1
lw $v0 0x0050 $zero
j 0x0000011
addi $v0 $zero 0x0001
sw $v0 0x0054 $zero
lui $t1, 12
addi $t0, $t0, 0x0054
addi $t8, $t8, $0
J 0x0000012
```

Part f

DATAPATH

```
module datapath (input logic clk, reset, memtoreg, branch, alusrc, regdst,
    input logic regwrite, jump, memwrite,
    input logic[2:0] alucontrol,
    output logic[31:0] pc,
    input logic[31:0] instr,
    output logic[31:0] aluout, writedata,
    input logic[31:0] readdata);

    logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
    logic [31:0] signimm, signimmsh, srca, srcb, result;
    //Pipe logic
    logic useless = 1'b1;
    logic stallD, stallF, pcplus4D, flushE, pcsrc,
        pcsrcE, regwriteE, memtoregE, memwriteE, alusrcE, regdstE,
        regwriteM, memtoregM, memwriteM,
        regwriteW, memtoregW,
        forwardAD, forwardBD;
    logic[31:0] instrD, source1E, source2E, signImmE,
        writeDataE, aluOutM, writeDataM,
        readDataW, aluOutW,
        srcaComp, srcbComp,
        srcAE, srcBE;
    logic[4:0] rsE, rtE, rdE, writeRegE, writeRegM, writeRegW;
    logic[2:0] alucontrolE;
    logic[1:0] forwardAE, forwardBE;

    //Branch Decision
    mux2 srcaMux(srca, aluOutM, forwardAD, srcaComp);
    mux2 srcbMux(srcb, aluOutM, forwardBD, srcbComp);
    assign pcsrc = branch & (srcaComp == srcbComp);

    // next PC logic
    flopr #(32) pcreg(clk, reset, ~stallF, pcnext, pc);
    adder    pcadd1(pc, 32'b100, pcplus4);
    sl2      immsh(signimm, signimmsh);
    adder    pcadd2(pcplus4D, signimmsh, pcbranch);
    mux2 pcbrmux(pcplus4, pcbranch, pcsrcE, pcnextbr);
    mux2 pcmux(pcnextbr, {pcplus4[31:28], instr[25:0], 2'b00}, jump, pcnext);

    //Hazard Unit
    hazard h(rsD, rtD, rsE, rtE, writeRegE, writeRegM,
        writeRegW, regwriteE, regwriteM, regwriteW,
        memtoregE, memtoregM, branch,
        forwardAD, forwardBD, forwardAE, forwardBE,
        stallF, stallD, flushE);

    //Pipe F-D
    pipeRegisterFD fdreg (clk, reset, ~stallD, (jump |
        pcsrcE), instr, pcplus4, instrD, pcplus4D);
```



```
//Pipe D-E
pipeRegisterDE dereg(clk,reset,useless,flushE,srcA,writedata,
    instr[25:21],instr[20:16],instr[15:11],
    signimm,source1E,source2E,rsE,rtE,rdE,signImmE,
    //Control Signals
    pcsrc,regwrite,memtoreg,memwrite,alucontrol,regdst,
    pcsrcE,regwriteE,memtoregE,memwriteE,alucontrolE,alusrcE,regdstE);
```

```
//Pipe E-M
pipeRegisterEM emreg(clk,reset,useless,~useless,aluOut,
    writeDataE,writeRegE,
    aluOutM,writeDataM,writeRegM,
    //Control Signals
    regwriteE,memtoregE,memwriteE,
    regwriteM,memtoregM,memwriteM);
```

```
//Pipe M-W
pipeRegisterMW mwreg(clk,reset,useless,~useless,
    readdata, aluOutM,writeRegM,
    readDataW,aluOutW,writeRegW,
    //Control Signals
    regwriteM,memtoregM,
    regwriteW,memtoregW);
```

```
// register file logic
regfile rf (clk, regwriteW, instrD[25:21], instrD[20:16], writeRegW,
    result, srcA, writedata);
mux3 alu1(source1E,result,aluOutM,forwardAE,srcAE);
mux3 alu2(source2E,result,aluOutM,forwardBE,writeDataE);
mux2p #(5) wrmux (rtE, rdE, regdstE, writeregE);
mux2p #(32) resmux (aluOutW, readDataW, memtoregW, result);
signext se (instr[15:0], signimm);
// ALU logic
mux2p #(32) srcbmux (writeDataE, signImmE, alusrcE, srcBE);
alu alu (srcAE, srcBE, alucontrolE, aluout);
```

```
endmodule
```

```
//2-to-1 MUX
module mux2(input logic[31:0] d0, d1,
    input logic s,
    output logic[31:0] y);
```

```
    assign y = s ? d1 : d0;
endmodule
```

```
//3-to-1 MUX
module mux3(input logic [31:0] d0,d1,d2,
    input logic [1:0] S,
    output logic [31:0] Y
);
```

```

assign Y = S[1] ? (S[0] ? 32'bX : d2)
: (S[0] ? d1 : d0);

```

```

endmodule

```

PIPELINE REGISTERS

```

//Pipe register between fetch and decode

```

```

module pipeRegisterFD

```

```

    (input logic clk, reset,en, clear,
     input logic[31:0] instrF,
     input logic[31:0] pcplus4F,
     output logic[31:0] instrD,
     output logic[31:0] pcplus4D);

```

```

    always_ff@(posedge clk, posedge reset)
    if (reset | clear) begin instrD <= 0; pcplus4D <= 0; end
    else if (en)      begin instrD <= instrF; pcplus4D <= pcplus4F; end
endmodule

```

```

//Pipe register between decode and execute

```

```

module pipeRegisterDE

```

```

    (input logic clk, reset,en, clear,
     input logic[31:0] source1D,source2D,
     input logic [4:0] rsD,rtD,rdD,
     input logic[31:0] signImmD,
     output logic[31:0] source1E,source2E,
     output logic[4:0] rsE,rtE,rdE,
     output logic[31:0] signImmE,
     //Control Signals
     input logic psrcD,
     input logic regwriteD,memtoregD,memwriteD,
     input logic[2:0] alucontrolD,
     input logic alusrcD, regdstD,
     output logic psrcE,
     output logic regwriteE,memtoregE,memwriteE,
     output logic[2:0] alucontrolE,
     output logic alusrcE, regdstE);

```

```

    always_ff@(posedge clk, posedge reset)
    if (reset | clear) begin
        source1E <= 0; source2E <= 0;
        rsE <= 0; rtE <= 0; rdE <= 0;
        signImmE <= 0;
        //Signals
        psrcE <= 0; regwriteE <= 0;
        memtoregE <= 0; memwriteE <= 0; alucontrolE <= 0;
        alusrcE <= 0; regdstE <= 0;
    end
    else if (en) begin
        source1E <= source1D; source2E <= source2D;
        rsE <= rsD; rtE <= rtD; rdE <= rdD;
    end

```

```

        signImmE <= signImmD;
        //Signals
        pcsrcE <= pcsrcD; regwriteE <= regwriteD;
        memtoregE <= memtoregD; memwriteE <= memwriteD; alucontrolE <=
alucontrolD;
        alusrcE <= alusrcD; regdstE <= regdstD;
        end
    endmodule

```

//Pipe register between execute and memory

```

module pipeRegisterEM
    (input logic clk, reset,en, clear,
        input logic[31:0] aluOutE,writeDataE,
        input logic [4:0] writeRegE,
        output logic[31:0] aluOutM,writeDataM,
        output logic[4:0] writeRegM,
        //Control Signals
        input logic regwriteE,memtoregE,memwriteE,
        output logic regwriteM,memtoregM,memwriteM);

    always_ff@(posedge clk, posedge reset)
        if (reset | clear) begin
            aluOutM <= 0; writeDataM <= 0;
            writeRegM <= 0;
            //Signals
            regwriteM <= 0; memtoregM <= 0; memwriteM <= 0;
            end
        else if (en) begin
            aluOutM <= aluOutE; writeDataM <= writeDataE;
            writeRegM <= writeRegE;
            //Signals
            regwriteM <= regwriteE; memtoregM <= memtoregE; memwriteM <=
memwriteE;
            end
    endmodule

```

//Pipe register between memory and writeback

```

module pipeRegisterMW
    (input logic clk, reset,en, clear,
        input logic[31:0] readDataM,
        input logic[31:0] aluOutM,
        input logic [4:0] writeRegM,
        output logic[31:0] readDataW,
        output logic[31:0] aluOutW,
        output logic[4:0] writeRegW,
        //Control Signals
        input logic regwriteM,memtoregM,
        output logic regwriteW,memtoregW);

    always_ff@(posedge clk, posedge reset)
        if (reset | clear) begin
            readDataW <= 0; aluOutW <= 0;

```

```

    writeRegW <= 0;
    //Signals
    regwriteW <= 0; memtoregW <= 0;
    end
else if (en) begin
    readDataW <= readDataM; aluOutW <= aluOutM;
    writeRegW <= writeRegM;
    //Signals
    regwriteW <= regwriteM; memtoregW <= memtoregM;
    end
endmodule

```

HAZARD UNIT

```

module hazard(input logic [4:0] rsD, rtD, rsE, rtE,
    input logic [4:0] writeregE, writeregM, writeregW,
    input logic regwriteE, regwriteM, regwriteW,
    input logic memtoregE, memtoregM, branchD,
    output logic forwardaD, forwardbD,
    output logic [1:0] forwardaE, forwardbE,
    output logic stallF, stallD, flushE);

    logic lwstallD, branchstallD;

    // forwarding sources to D stage (branch equality)
    assign forwardaD = (rsD != 0 & rsD == writeregM & regwriteM);
    assign forwardbD = (rtD != 0 & rtD == writeregM & regwriteM);

    // forwarding sources to E stage (ALU)
    always_comb
    begin
        forwardaE = 2'b00; forwardbE = 2'b00;
        if (rsE != 0)
            if (rsE == writeregM & regwriteM)
                forwardaE = 2'b10;
            else if (rsE == writeregW & regwriteW)
                forwardaE = 2'b01;
        if (rtE != 0)
            if (rtE == writeregM & regwriteM)
                forwardbE = 2'b10;
            else if (rtE == writeregW & regwriteW)
                forwardbE = 2'b01;
    end

    // stalls
    assign #1 lwstallD = memtoregE &
        (rtE == rsD | rtE == rtD);
    assign #1 branchstallD = branchD &
        (regwriteE &
        (writeregE == rsD | writeregE == rtD) |
        memtoregM &
        (writeregM == rsD | writeregM == rtD));
    assign #1 stallD = lwstallD | branchstallD;
    assign #1 stallF = stallD;

```

```
// stalling D stalls all previous stages
assign #1 flushE = stallD;
// stalling D flushes next stage
// Note: not necessary to stall D stage on store
// if source comes from load;
// instead, another bypass network could
// be added from W to M
endmodule
```

CONTROLLER

```
module controller(input  logic[5:0] op, funct,
                  output logic  memtoreg, memwrite,
                  output logic  branch, alusrc,
                  output logic  regdst, regwrite,
                  output logic  jump,
                  output logic[2:0] alucontrol);

    logic [1:0] aluop;

    maindec md (op, memtoreg, memwrite, branch, alusrc, regdst, regwrite,
                jump, aluop);

    aludec ad (funct, aluop, alucontrol);

endmodule
```

MIPS PIPELINED PROCESSOR

```
// single-cycle MIPS processor, with controller and datapath
module mips (input  logic      clk, reset,
             output logic[31:0] pc,
             input  logic[31:0] instr,
             output logic      memwrite,
             output logic[31:0] aluout, writedata,
             input  logic[31:0] readdata);

    logic      memtoreg, pcsrc, alusrc, regdst, regwrite, jump;
    logic [2:0] alucontrol;

    controller c (instr[31:26], instr[5:0], memtoreg, memwrite, pcsrc,
                  alusrc, regdst, regwrite, jump, alucontrol);

    datapath dp (clk, reset, memtoreg, pcsrc, alusrc, regdst, regwrite, jump,
                 memwrite,
                 alucontrol, pc, instr, aluout, writedata, readdata);

endmodule
```

```
module maindec (input logic[5:0] op,
                output logic memtoreg, memwrite, branch,
                output logic alusrc, regdst, regwrite, jump,
```

```

        output logic[1:0] aluop );
    logic [8:0] controls;

    assign {regwrite, regdst, alusrc, branch, memwrite,
            memtoreg, aluop, jump} = controls;
    always_comb
    case(op)
        6'b000000: controls <= 9'b110000100; // R-type
        6'b100011: controls <= 9'b101001000; // LW
        6'b101011: controls <= 9'b001010000; // SW
        6'b000100: controls <= 9'b000100010; // BEQ
        6'b001000: controls <= 9'b101000000; // ADDI
        6'b000010: controls <= 9'b000000001; // J
        default: controls <= 9'bxxxxxxx; // illegal op
    endcase
endmodule

```

ALUDECODER

```

module aludec (input logic[5:0] funct,
               input logic[1:0] aluop,
               output logic[2:0] alucontrol);
    always_comb
    case(aluop)
        2'b00: alucontrol = 3'b010; // add (for lw/sw/addi)
        2'b01: alucontrol = 3'b110; // sub (for beq)
        default: case(funct) // R-TYPE instructions
            6'b100000: alucontrol = 3'b010; // ADD
            6'b100010: alucontrol = 3'b110; // SUB
            6'b100100: alucontrol = 3'b000; // AND
            6'b100101: alucontrol = 3'b001; // OR
            6'b101010: alucontrol = 3'b111; // SLT
            default: alucontrol = 3'bxxx; // ???
        endcase
    endcase
endmodule

```

```

module regfile (input logic clk, we3,
               input logic[4:0] ra1, ra2, wa3,
               input logic[31:0] wd3,
               output logic[31:0] rd1, rd2);

    logic [31:0] rf [31:0];
    // three ported register file: read two ports combinationaly
    // write third port on rising edge of clock. Register0 hardwired to 0.

```

```

    always_ff@(posedge clk, posedge we3)
        if (we3)
            rf [wa3] <= wd3;
    assign rd1 = (ra1 != 0) ? rf [ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf [ra2] : 0;
endmodule

```

ALU

```

module alu(input logic [31:0] A, B,
          input logic [2:0] F,
          output logic [31:0] Z);
    logic [31:0] Y;
    always_comb
        case (F)
            3'b000: Y = A & B;
            3'b001: Y = A | B;
            3'b010: Y = A + B;
            3'b100: Y = A & ~B;
            3'b101: Y = A | ~B;
            3'b110: Y = A - B;
            3'b111: Y = (A < B) + 32'b0000;
        endcase
    assign Z = Y;
endmodule

```

ADDER

```

module adder (input logic[31:0] a, b,
              output logic[31:0] y);

    assign y = a + b;
endmodule

```

```

module sl2 (input logic[31:0] a,
            output logic[31:0] y);

    assign y = {a[29:0], 2'b00}; // shifts left by 2
endmodule

```

```

module signext (input logic[15:0] a,
                 output logic[31:0] y);

    assign y = {{16{a[15]}}, a}; // sign-extends 16-bit a
endmodule

```

D FLIP-FLOP

```

// parameterized register
module flopr #(parameter WIDTH = 8)
    (input logic clk, reset, en,
     input logic[WIDTH-1:0] d,
     output logic[WIDTH-1:0] q);

    always_ff@(posedge clk, posedge reset)
        if (reset) q <= 0;
        else if (en) q <= d;
endmodule

```

MUX 2-1

```

// paramaterized 2-to-1 MUX
module mux2p #(parameter WIDTH = 8)
    (input logic[WIDTH-1:0] d0, d1,
     input logic s,

```

```

        output logic[WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

```

TOP

```

module top (input logic      clk, reset,
            output logic[31:0] writedata, dataadr,
            output logic      memwrite);

    logic [31:0] pc, instr, readdata;

    // instantiate processor and memories
    mips mips (clk, reset, pc, instr, memwrite, dataadr, writedata, readdata);
    imem imem (pc[7:2], instr);
    dmem dmem (clk, memwrite, dataadr, writedata, readdata);
endmodule

```

TEST BENCH

```

module testbench();
    reg clk;
    reg rst;
    reg [31:0] writeData;
    reg [31:0] dataAddress;
    reg memWrite;

    top proc(clk,rst,writeData,dataAddress,memWrite);

    always
        #5 clk = ~clk;
    initial
    begin
        // time = 0
        clk = 1'b0;
        // Reset CPU
        rst = 1'b1;
        // run 1st iteration to reset cpu, and load first instruction
        @(posedge clk);

        // set Rest to 0
        rst = 1'b0;

        // Run through 5 CPU cycles
        repeat(40)
            @(posedge clk);

        $finish();
    end
endmodule

```